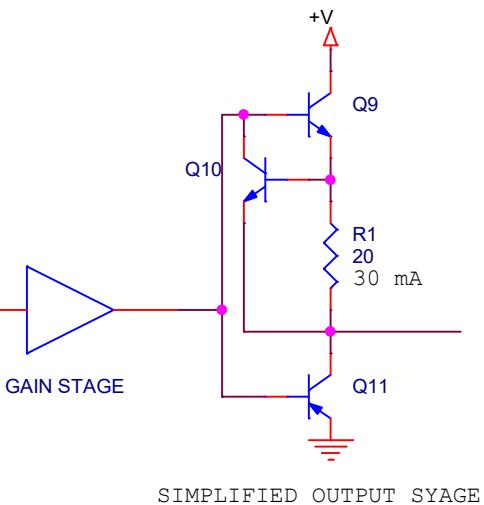
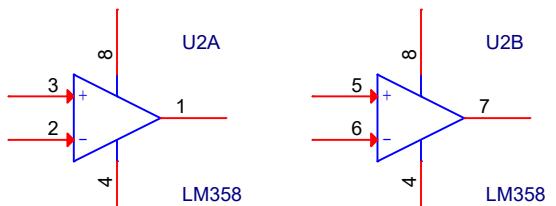


LM158 - Military / aerospace
 LM258 - Industrial grade
 LM358 - Commercial grade
 LM2904 - same thing
 LM324 or LM2902 - Quad package



Simplified internals.
 The PNP input design allows the input voltages to work well close to ground with +V only power.



(Assumed power, +5 V)
 Input offset voltage = 3 mV
 Input bias current = 45 nA
 Input offset current = 5 nA
 Input voltage range = 0 V to (VCC - 1.5 V) <<< !!
 Supply current = 0.5 mA
 Large signal voltage gain = 100 V/mV
 Common mode rejection = 85 dB
 Power supply rejection = 100 dB
 Output current = 20 mA
 Output voltage range = 0 V to (VCC - 1.5 V) <<< !!
 Unity gain bandwidth = 1 MHz

<<<!! Why use the LM358 instead of LM741

Title	
G25647, Basic op amps, LM358	
Size A	Document Number Design 1412
Rev 1	

Date: Monday, April 05, 2021

Sheet 1 of 1